

كلية مدينة العلم الجامعة

قسم هندسة الحاسوب

محاضرات المرحلة الاولى لمادة الهندسة الالكترونية

اعداد

د. سعيد سلمان كمون

# المحاضرة الرابعة

Solved Problems

اسئلة محلولة

Electronic Devices and Circuit Theory


Eleventh Edition

Robert L. Boylestad and Louis Nashelsky

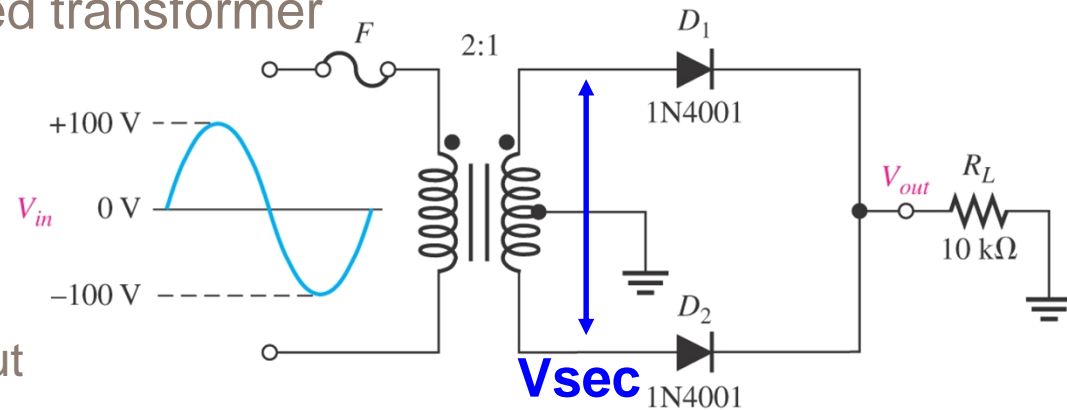
# Full-wave Rectifier - Example

- Assuming a center-tapped transformer

- Find the turns ratio
- Find  $V_{sec}$
- Find  $V_{out}$
- Find PIV
- Draw the  $V_{sec}$  and  $V_{out}$
- What is the output freq?




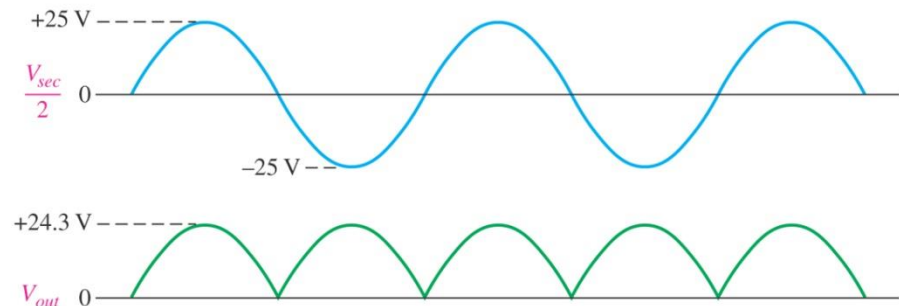- $n=1:2=0.5$
- $V_{sec}=n*V_{pri}=25$
- $V_{out} = V_{sec}/2 - 0.7$
- $PIV = V_{sec}-0.7=24.3 \text{ V}$


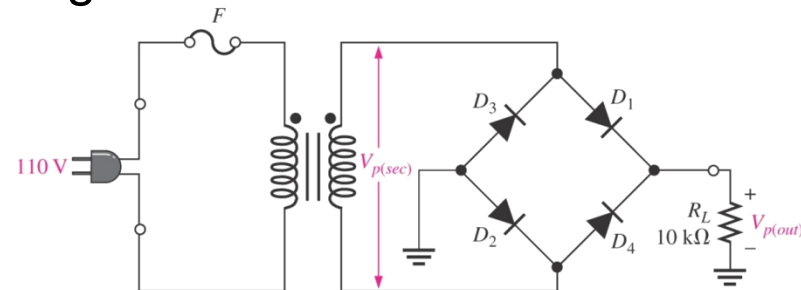
# Bridge Full-wave Rectifier

- Uses an untapped transformer → larger  $V_{sec}$
- Four diodes connected creating a bridge
  - When positive voltage →
    - D1 and D2 are forward biased
  - When negative voltage →
    - D3 and D4 are forward biased
- Two diodes are always in series with the load
  - $V_{p(out)} = V_{p(sec)} - 1.4V$
  - The negative voltage is inverted
- The Peak Inverse Voltage (PIV)
  - $PIV = V_{p(out)} + 0.7$



# Bridge Full-wave Rectifier - Example


- Assume 12 Vrms secondary voltage for the standard 120 Vrms across the primary
  - Find the turns ratio
  - Find  $V_p(\text{sec})$
  - Show the signal direction when  $V_{in}$  is positive
  - Find PIV rating

$$n = V_{\text{sec}} / V_{\text{pri}} = 0.1 \rightarrow 10:1$$

$$V_p(\text{sec}) = (0.707)^{-1} \times V_{\text{rms}} = 1.414(12) = 17 \text{ V}$$

$$V_p(\text{out}) = V(\text{sec}) - (0.7 + 0.7) = 15.6 \text{ V through } D_1 \& D_2$$
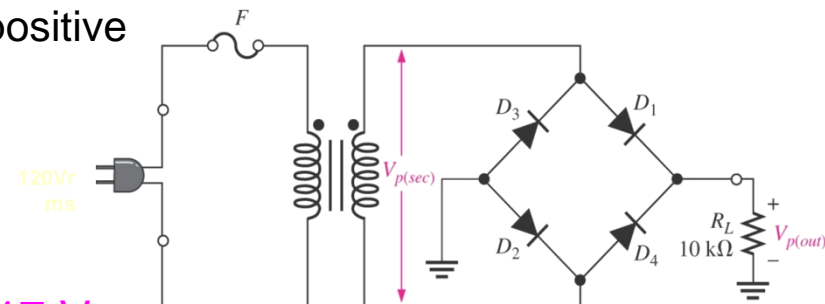
$$\text{PIV} = V_p(\text{out}) + 0.7 = 16.3 \text{ V}$$





Note:  $V_p - V_{br}$  ; hence, always convert from rms to  $V_p$

# Bridge Full-wave Rectifier - Comparison

	Half-wave	Full-wave	Bridge
Number of diodes	1	2	4
Rectifier input	$V_{p(2)}$	$0.5V_{p(2)}$	$V_{p(2)}$
DC output (ideal)	$V_{p(2)}$	$0.5V_{p(2)}$	$V_{p(2)}$
DC output (2d)	$V_{p(2)} - 0.7 \text{ V}$	$0.5V_{p(2)} - 0.7 \text{ V}$	$V_{p(2)} - 1.4 \text{ V}$
Ripple frequency	$f_{in}$	$2f_{in}$	$2f_{in}$
PIV	$2V_{p(2)}$	$V_{p(2)}$	$V_{p(2)}$
Diode current	$I_{dc}$	$0.5I_{dc}$	$0.5I_{dc}$

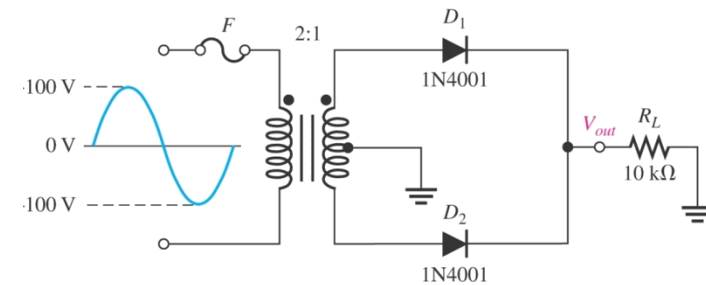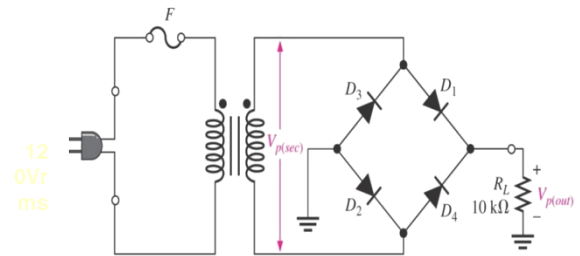$V_p(2)$ =Peak secondary voltage ;  $V_p(out)$  Peak output voltage ;  $I_{dc}$  = dc load current



**Make sure you understand this!**

# Diode clipper

- What is  $V_{out}$ ?



- $V_{out}^+ = V_{in} (R_L)/(R_L+R_1) = 9.09$

- $V_{out}^- = -0.7$

Forward biased when positive

Reverse biased when negative,  
hence voltage drop is only -0.7

So how can we change the offset?

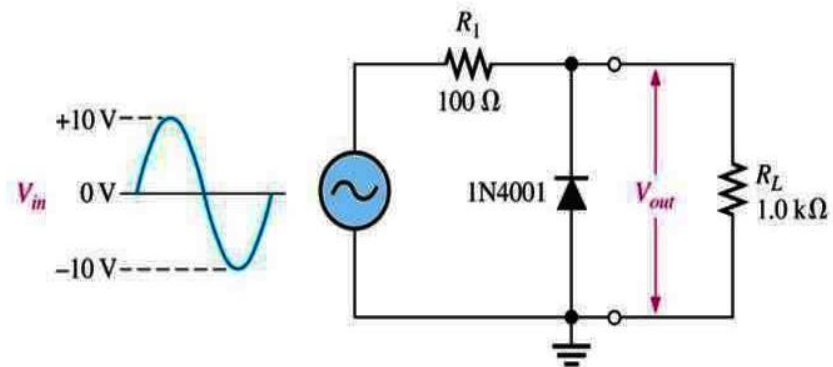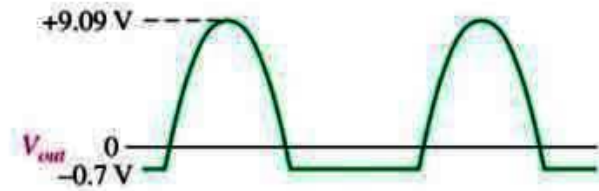



# Full-Wave Rectification

The rectification process can be improved by using a full-wave rectifier circuit.

Full-wave rectification produces a greater DC output:


Half-wave:  $V_{dc} = 0.318 V_m$

Full-wave:  $V_{dc} = 0.636 V_m$

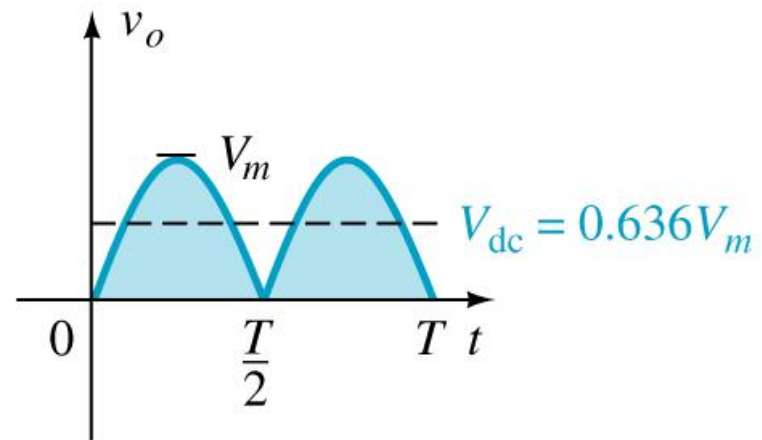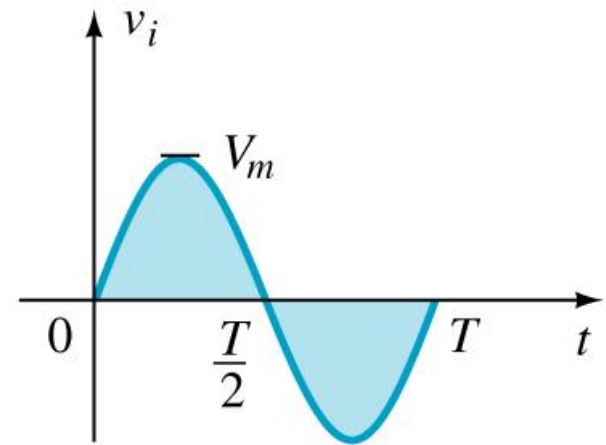




# Full-Wave Rectification

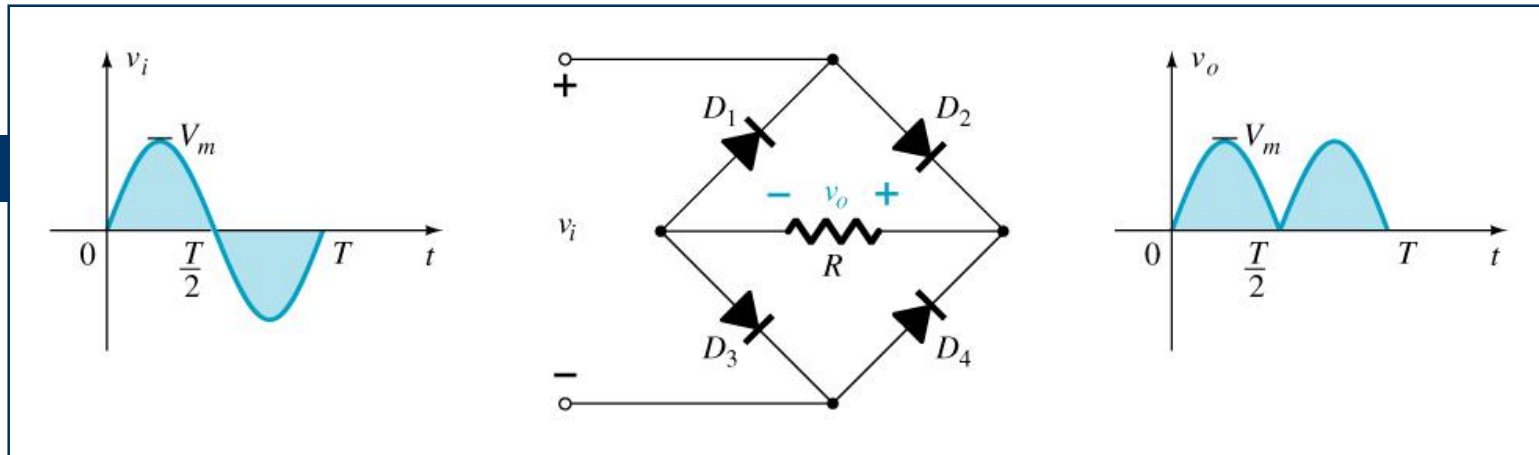


## Bridge Rectifier

A full-wave rectifier with four diodes that are connected in a bridge configuration

$$V_{DC} = 0.636 V_m$$

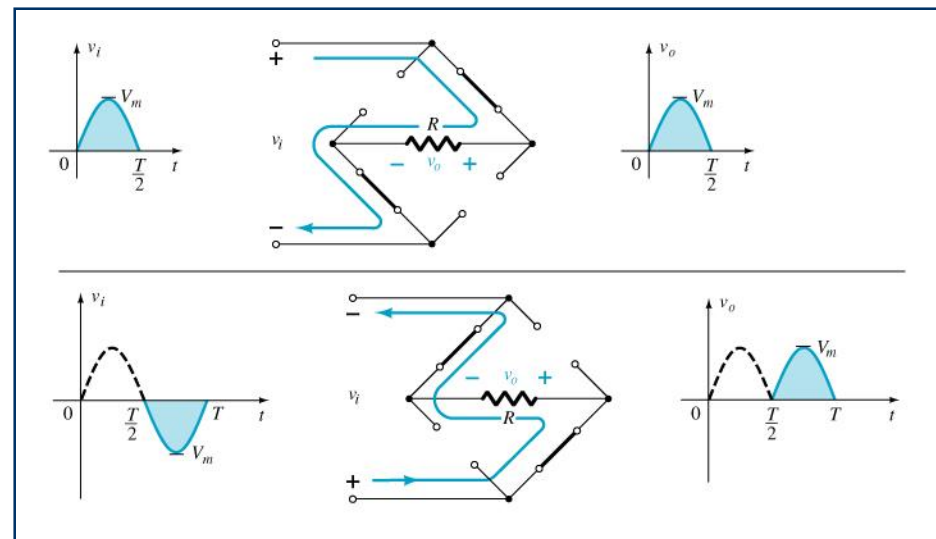


# Full-Wave Rectification

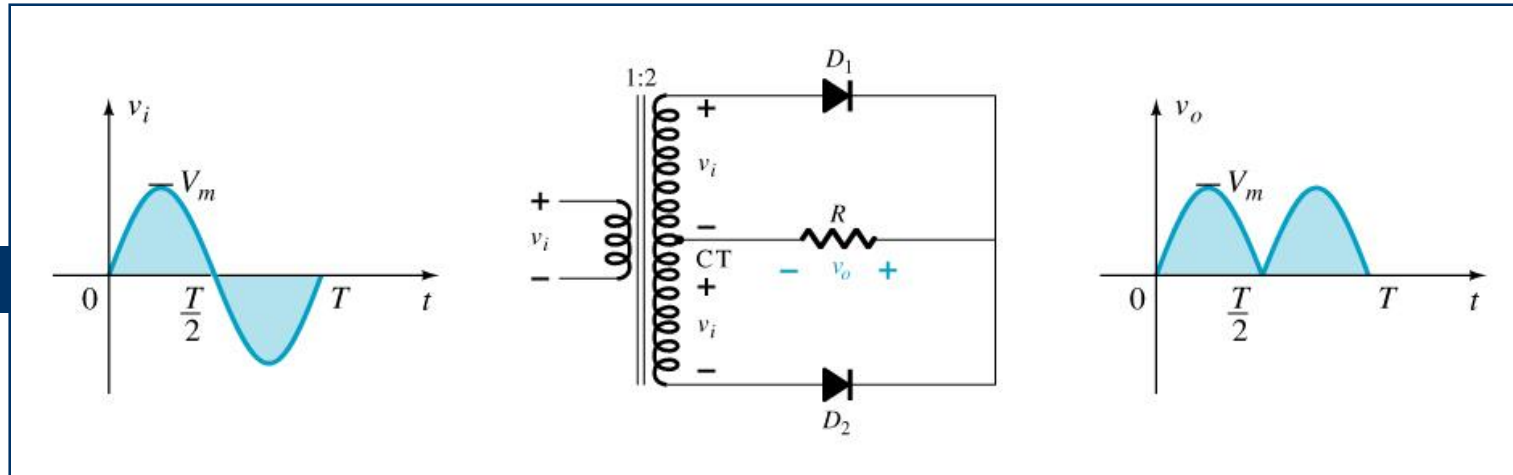

## Center-Tapped Transformer Rectifier

Requires two diodes and a center-tapped transformer

$$V_{DC} = 0.636 V_m$$

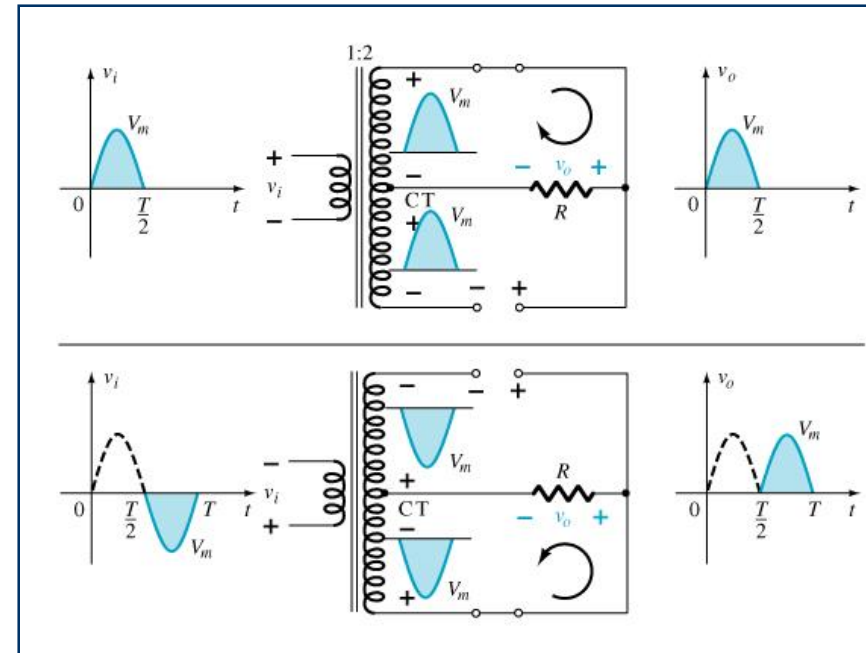

# Summary of Rectifier Circuits

In the center tapped transformer rectifier circuit, the peak AC voltage is the transformer secondary voltage to the tap.

Rectifier	Ideal $V_{DC}$	Realistic $V_{DC}$
Half Wave Rectifier	$V_{DC} = 0.318 V_m$	$V_{DC} = 0.318 V_m - 0.7$
Bridge Rectifier	$V_{DC} = 0.636 V_m$	$V_{DC} = 0.636 V_m - 2(0.7 \text{ V})$
Center-Tapped Transformer Rectifier	$V_{DC} = 0.636 V_m$	$V_{DC} = 0.636 V_m - 0.7 \text{ V}$

$V_m$  = the peak AC voltage