

كلية مدينة العلم الجامعة

قسم هندسة الحاسوب

محاضرات المرحلة الاولى لمادة الهندسة الالكترونية

اعداد

د. سعيد سلمان كمون

المحاضرة الخامسة

THE CLIPPER


Electronic Devices and Circuit Theory

Eleventh Edition

Robert L. Boylestad and Louis Nashelsky

Diode clipper – Changing the offset


Negative limiter

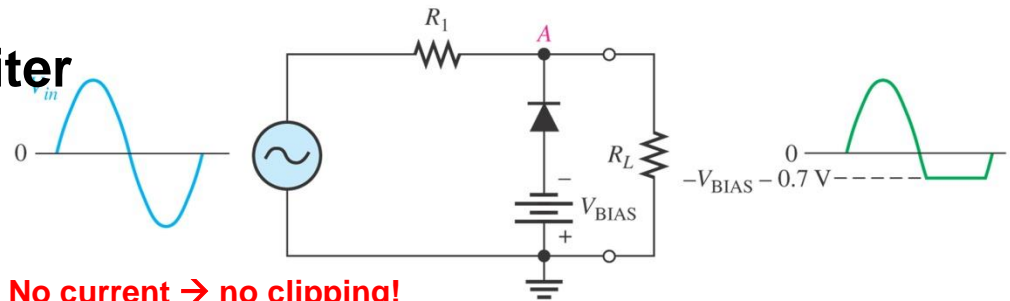

Remember:

When positive voltage \rightarrow reverse biased \rightarrow No current \rightarrow no clipping!


Positive limiter

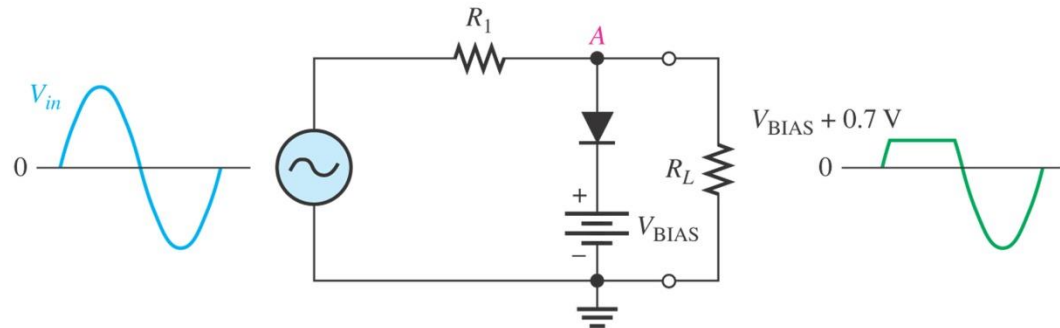

What if we mix these together?

Diode clipper

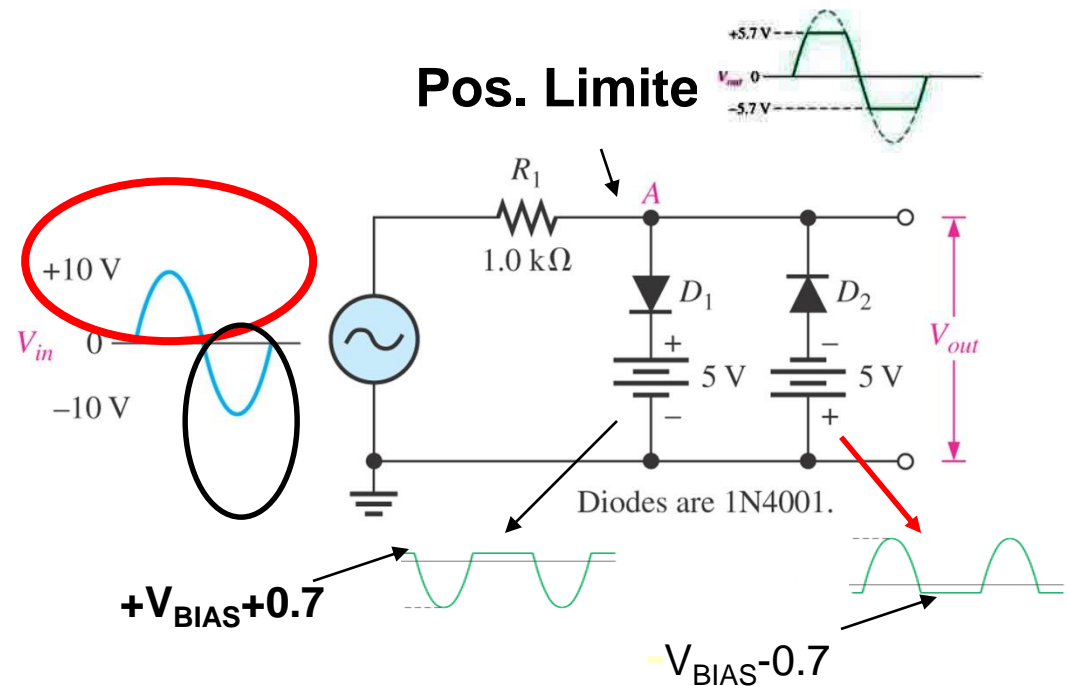
- When the input signal is positive D_1 is forward biased; acting as positive clipper



Diode Clippers




The diode in a series clipper “clips” any voltage that does not forward bias it:

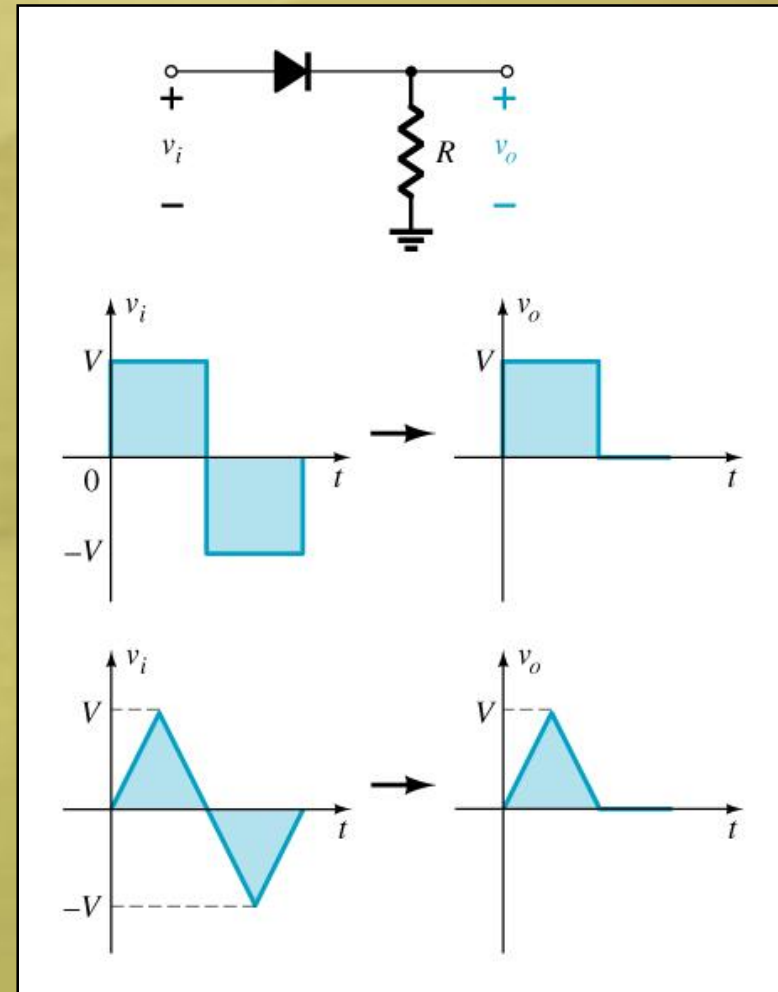- A reverse-biasing polarity
- A forward-biasing polarity less than 0.7 V (for a silicon diode)



Biased Clippers

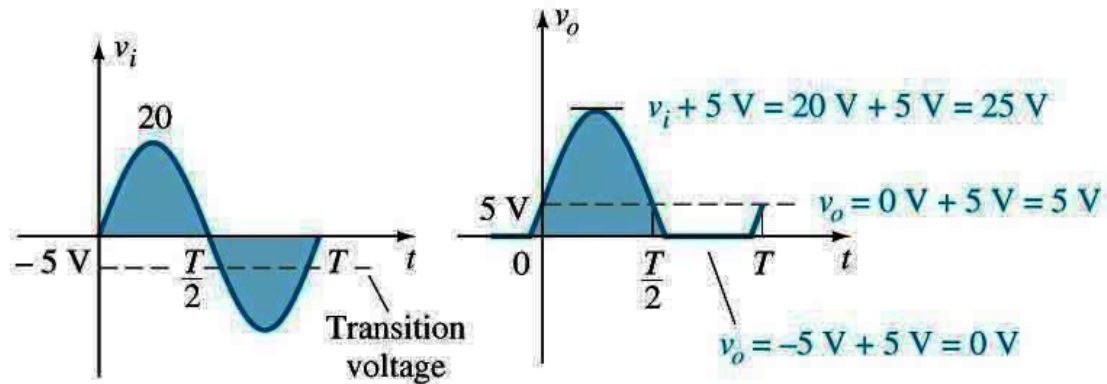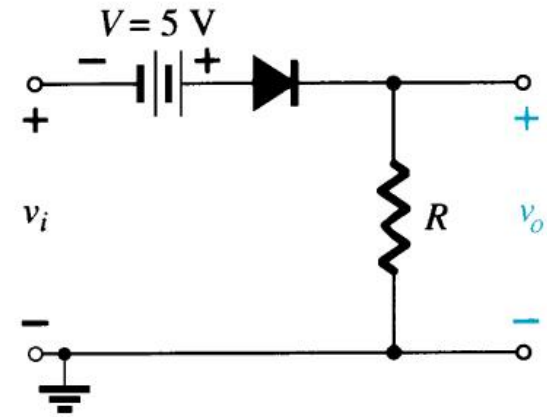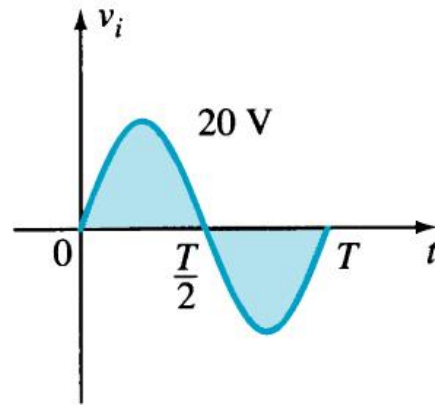
Adding a DC source in series with the clipping diode changes the effective forward bias of the diode.



Parallel Clippers

The diode in a parallel clipper circuit “clips” any voltage that forward biases it.

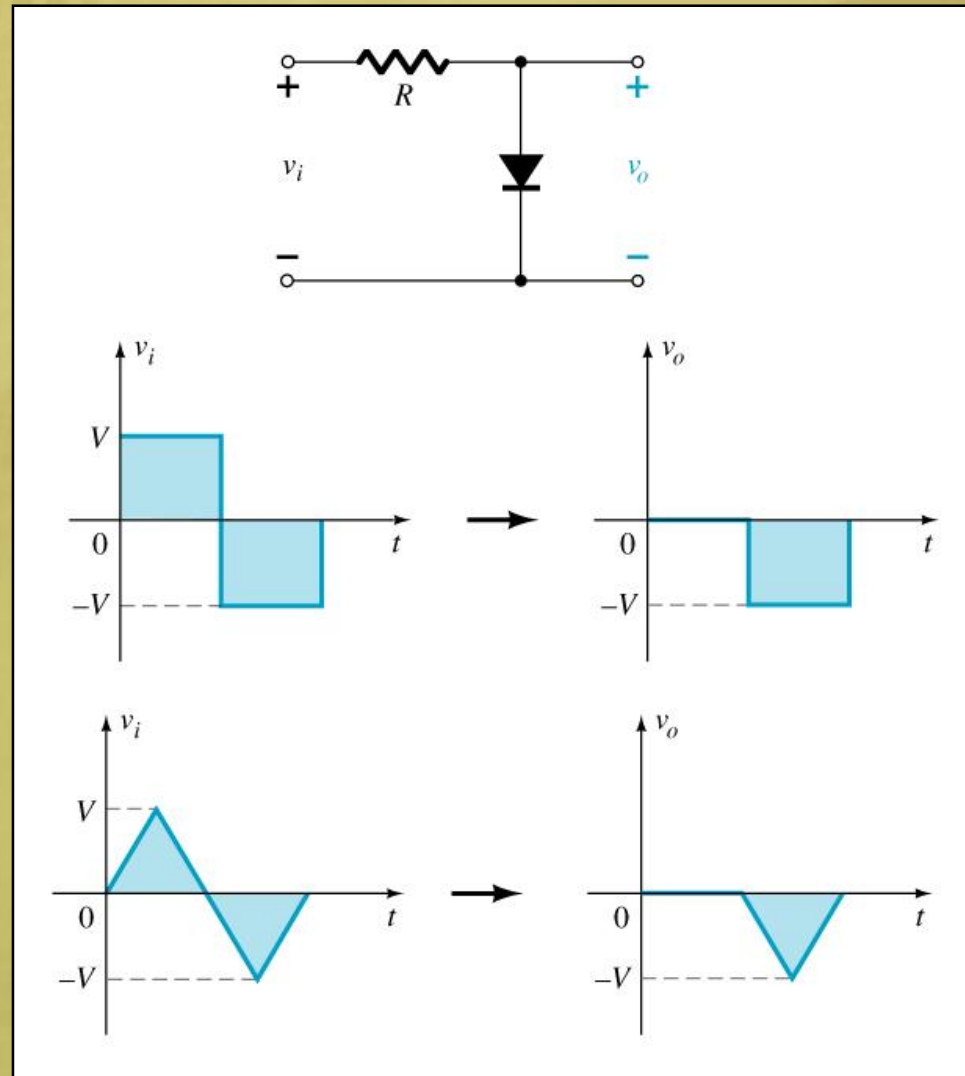
DC biasing can be added in series with the diode to change the clipping level.




Summary of Clipper Circuits

Simple Series Clippers (Ideal Diodes)





POSITIVE

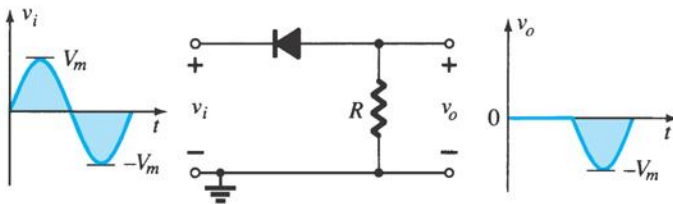

NEGATIVE


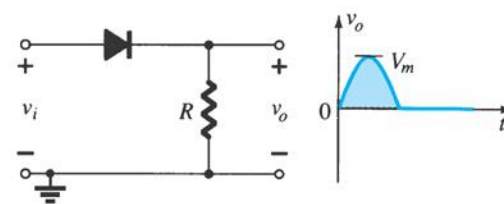


Biased Series Clippers (Ideal Diodes)


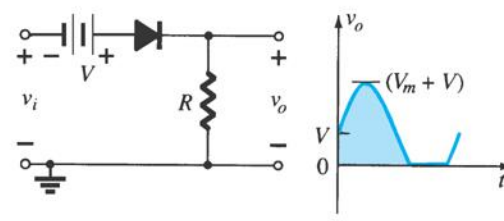
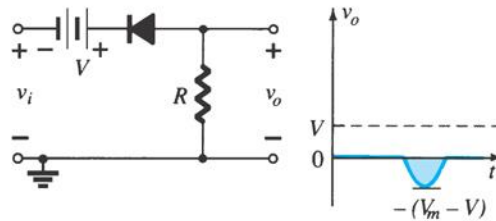
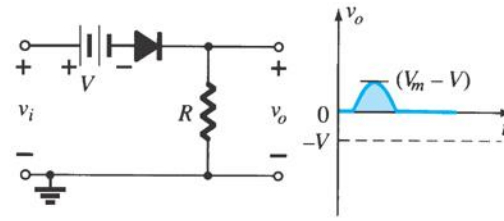
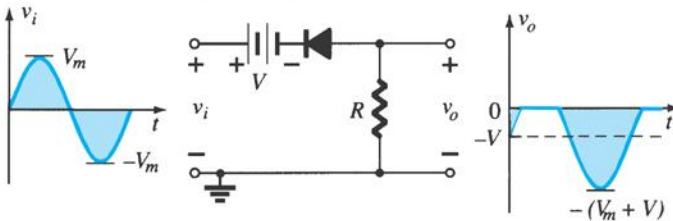


Summary of Clipper Circuits

Simple Parallel Clippers (Ideal Diodes)

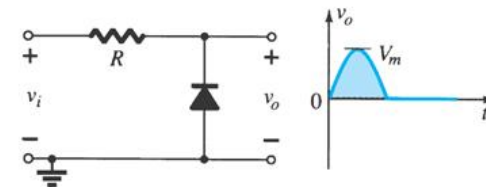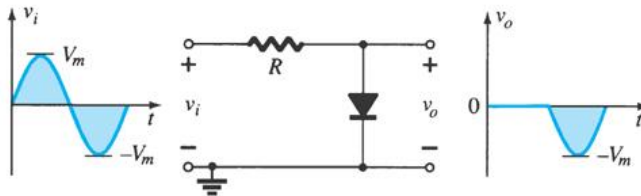


Biased Parallel Clippers (Ideal Diodes)

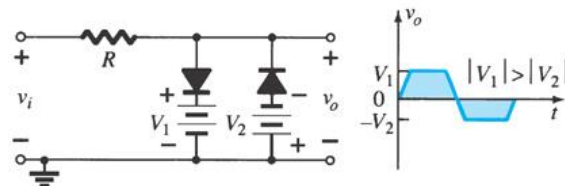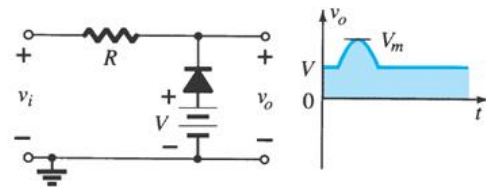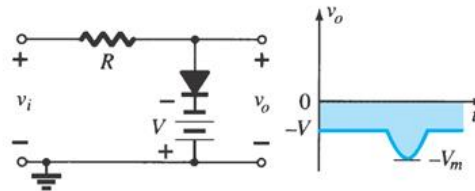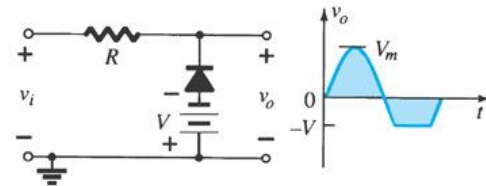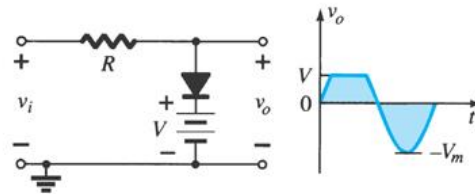


Summary of Clipper Circuits

Simple Series Clippers (Ideal Diodes)





POSITIVE

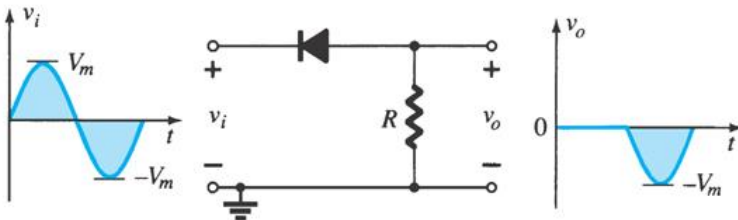

NEGATIVE


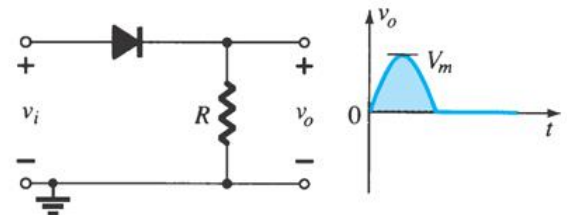


Biased Series Clippers (Ideal Diodes)

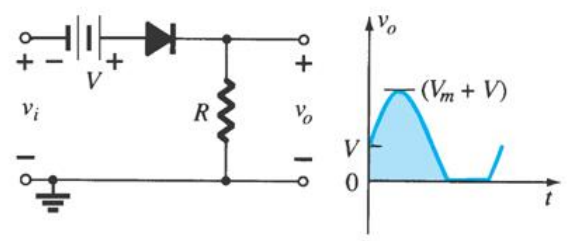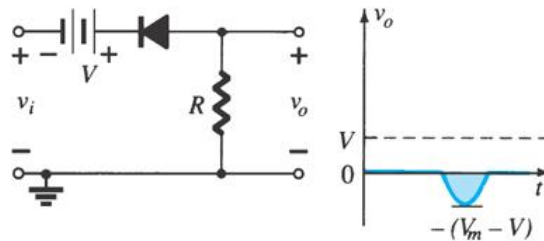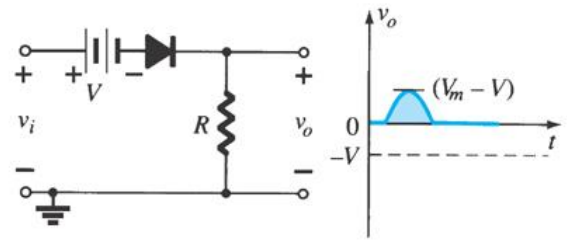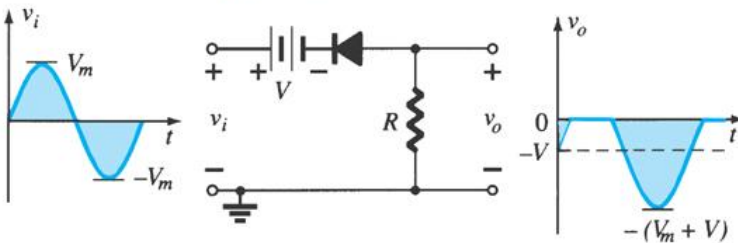


Clampers

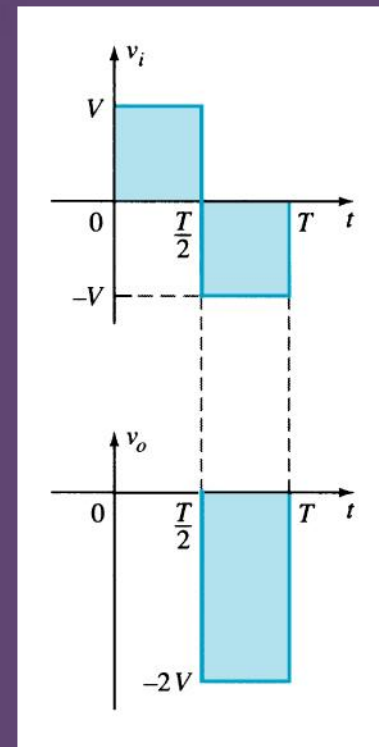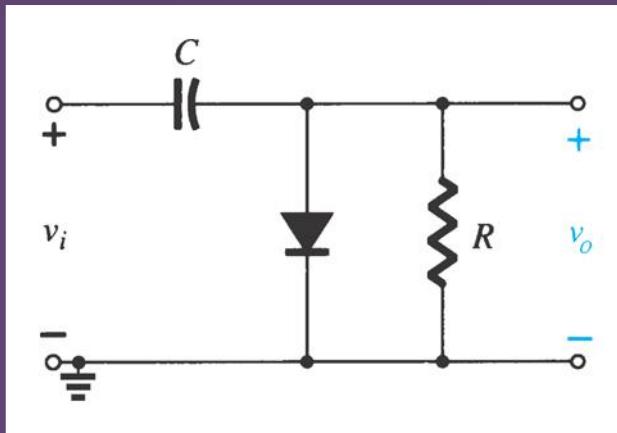A diode and capacitor can be combined to “clamp” an AC signal to a specific DC level.




Biased Clamper Circuits

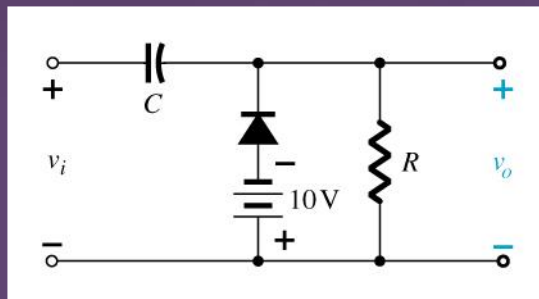The input signal can be any type of waveform such as a sine, square, or triangle wave.




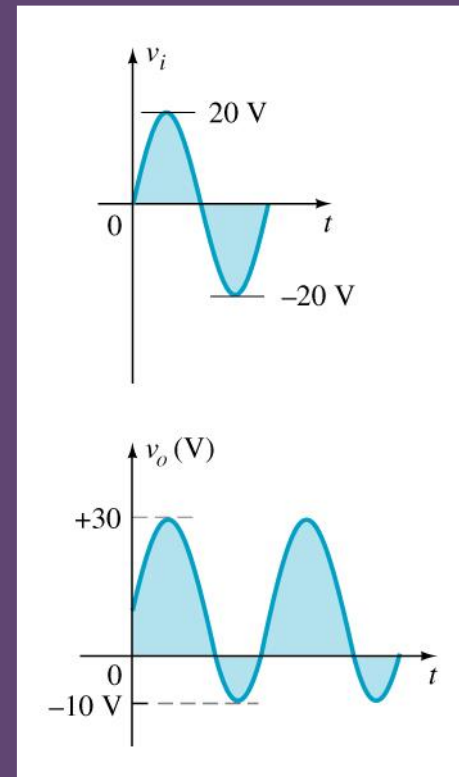The DC source lets you adjust the DC clamping level.



Summary of Clamper Circuits

Clamping Networks

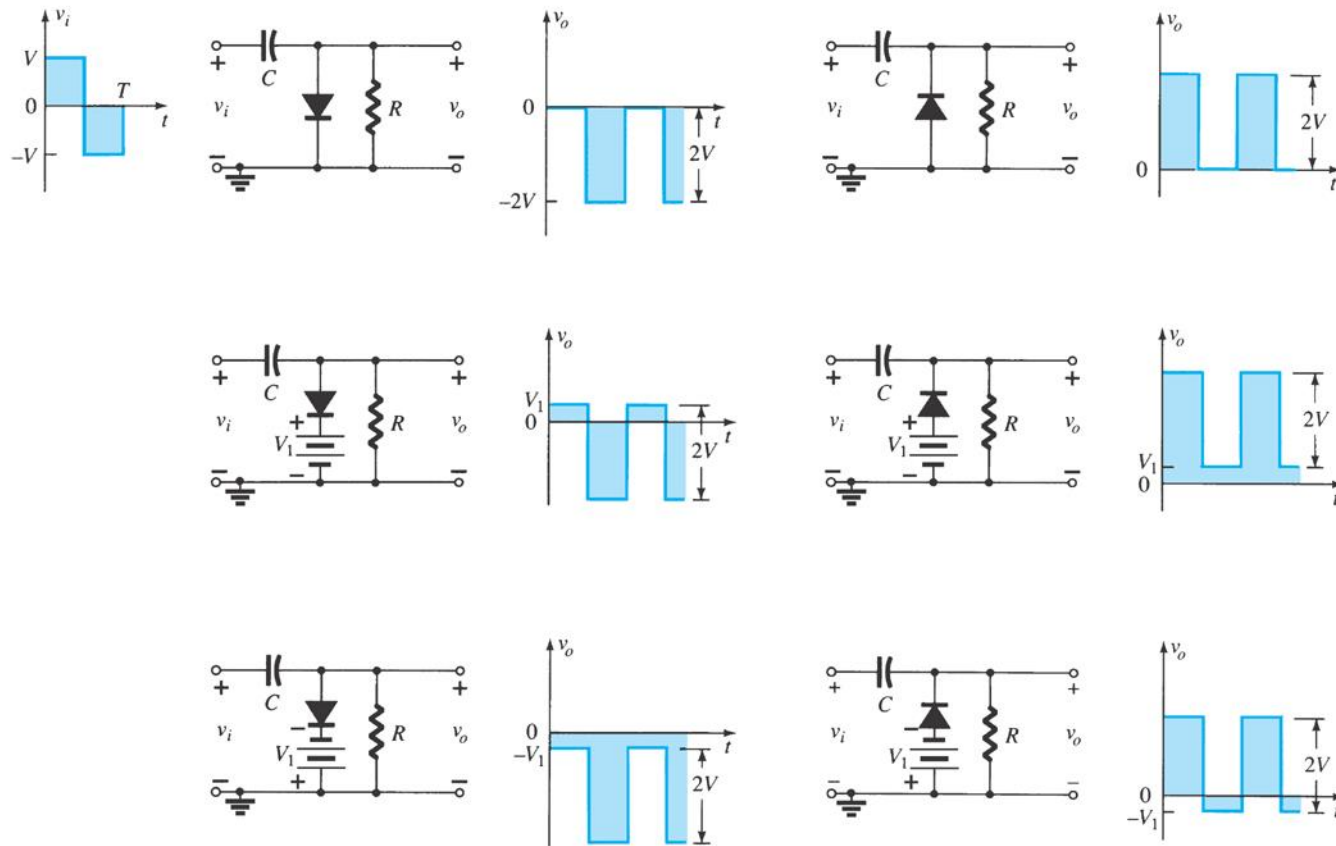

Zener Diodes



The Zener is a diode that is operated in reverse bias at the Zener Voltage (V_Z).

When $V_i \geq V_Z$

- The Zener is on
- Voltage across the Zener is V_Z
- Zener current: $I_Z = I_R - I_{RL}$
- The Zener Power: $P_Z = V_Z I_Z$

When $V_i < V_Z$

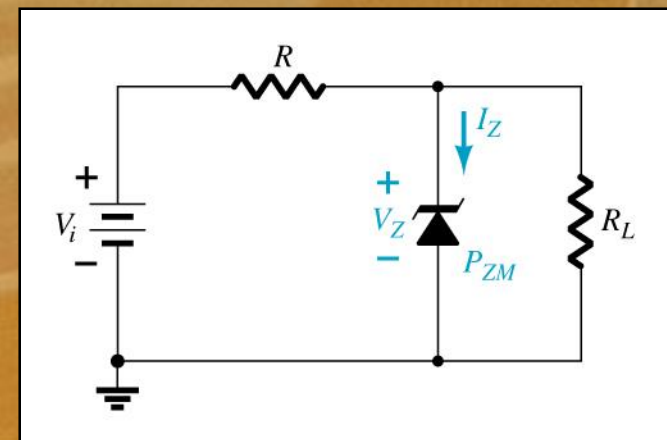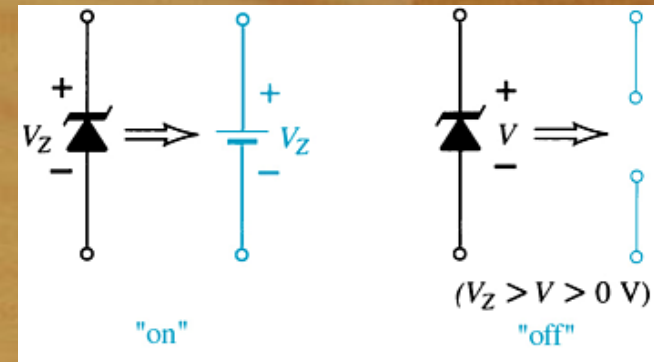- The Zener is off
- The Zener acts as an open circuit




Zener Resistor Values

If R is too large, the Zener diode cannot conduct because $I_Z < I_{ZK}$. The minimum current is given by:

$$I_{Lmin} = I_R - I_{ZK}$$

The *maximum* value of resistance is:

$$R_{Lmax} = \frac{V_Z}{I_{Lmin}}$$

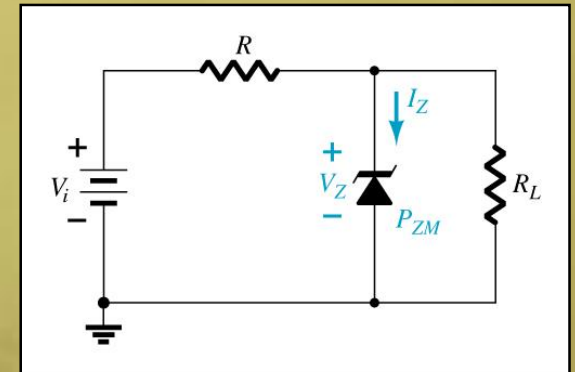

If R is too small, $I_Z > I_{ZM}$. The maximum allowable current for the circuit is given by:

$$I_{Lmax} = \frac{V_L}{R_L} = \frac{V_Z}{R_{Lmin}}$$

The *minimum* value of resistance is:

$$R_{Lmin} = \frac{RV_Z}{V_i - V_Z}$$

Voltage-Multiplier Circuits


Voltage multiplier circuits use a combination of diodes and capacitors to step up the output voltage of rectifier circuits. Three common voltage multipliers are the:

Voltage Doubler

Voltage Tripler

Voltage Quadrupler

Voltage Doubler

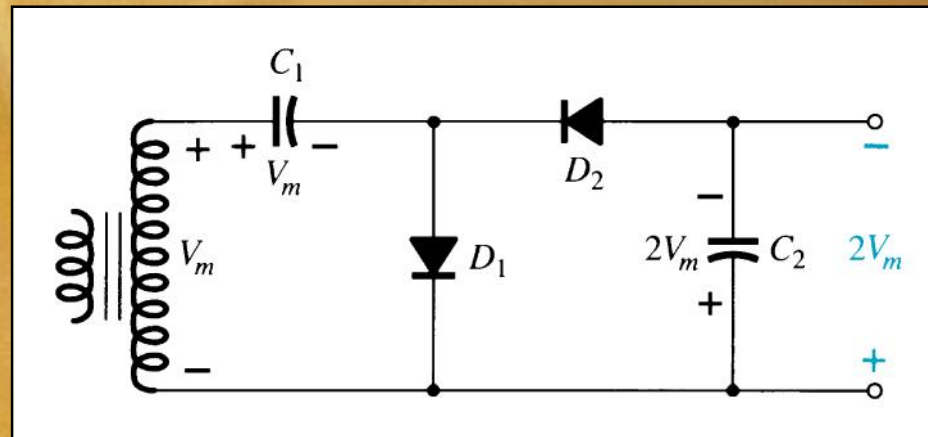

This half-wave voltage doubler's output can be calculated using:

$$V_{out} = V_{C2} = 2V_m$$

where V_m = peak secondary voltage of the transformer

Voltage Doubler

Positive Half-Cycle

D_1 conducts


D_2 is switched off

Capacitor C_1 charges to V_m
 D_1 is switched off

Negative Half-Cycle

D_2 conducts

$$V_{\text{out}} = V_{C_2} = 2V_m$$

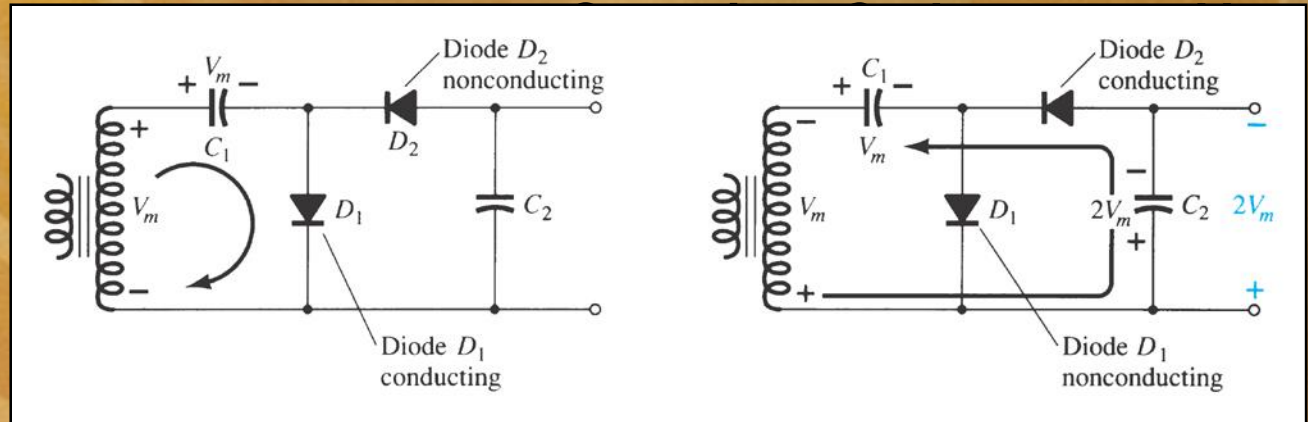

Voltage Tripler and Quadrupler

